

第二十二章：恒定电流 (2003年 - 2017年)

选择题

①  $L_1: P = \frac{V^2}{R}$        $L_2: P = \frac{V^2}{R}$   
 $40 = \frac{110^2}{R}$        $100 = \frac{110^2}{R}$   
 $R = 302.5 \Omega$        $R = 121 \Omega$

$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$   
 $\frac{1}{R} = \frac{1}{302.5} + \frac{1}{121}$   
 $R = 86.42 \Omega$  #

B

②  $I = nAve$   
 D.

③  $R = \rho \frac{l}{A}$   
 $20 = 4.4 \times 10^{-7} \times \frac{l}{\pi(1 \times 10^{-4})^2}$   
 $l = 1.43 \text{ m}$  #

C

④  $V = IR$        $V = IR$   
 $= 2 \times 3$        $6 = I \times 6$   
 $= 6V$        $I = 1A$  #

$V = IR$        $V = V_1 + V_2 + V_3$   
 $= (2+1) \times (2+1)$        $= 9V + 6V$   
 $= 9V$        $= 15V$  #

B

⑤ ①  $V = IR$       ③  $V = IR$   
 $V = I(10+20)$        $V = I'(\frac{20}{R+20} + 10)$   
 $I = \frac{V}{30}$        $I' = \frac{2V}{30(\frac{20R}{R+20} + 10)}$   
 $15 = \frac{20R + 10R + 200}{R+20}$

②  $\frac{1}{R'} = \frac{1}{R_1} + \frac{1}{R_2}$        $15R + 300 = 30R + 200$   
 $\frac{1}{R'} = \frac{1}{20} + \frac{1}{R}$        $R = \frac{20}{3} \Omega$  #  
 $R' = \frac{20R}{R+20}$

C

⑥

⑦  $R_I = \rho \frac{l}{A}$        $R_{II} = \frac{\rho \times l/4}{\pi(r/2)^2}$   
 $= \rho \times \frac{l}{\pi r^2}$        $= \frac{\rho l}{\pi r^2}$   
 $= \frac{\rho l}{\pi r^2}$

$R_{III} = \frac{\rho \times l/2}{\pi(r/2)^2}$        $R_{IV} = \frac{\rho \times l}{\pi(\frac{r}{2})^2}$   
 $= \frac{2\rho l}{\pi r^2}$        $= \frac{4\rho l}{\pi r^2}$

$R_V = \frac{\rho \times 5l}{\pi(2r)^2}$        $R_I = R_{II} < R_V < R_{III} < R_{IV}$   
 $= \frac{5\rho l}{4\pi r^2}$

⑧  $P = \frac{V^2}{R}$        $E = Pt$   
 $= \frac{120^2}{14}$        $= 1028.57 \times 5$   
 $= 1028.57 \text{ W}$        $= 5.14 \text{ kWh}$

$5.14 \text{ kWh} \times 0.05 = 0.26 \text{ #}$

D

⑨  $R = \rho \frac{l}{A}$        $R' = \rho \frac{l/2}{A}$   
 $= \frac{1}{2} \frac{\rho l}{A}$

$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$   
 $\frac{1}{R_T} = \frac{2A}{\rho l} + \frac{2A}{\rho l}$   
 $R_T = \frac{1}{4} \frac{\rho l}{A}$   
 $= \frac{1}{4} R$  #

A

⑩  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$   
 $\frac{1}{R} = \frac{1}{10} + \frac{1}{5} + \frac{1}{10}$   
 $R = 2.5 \Omega$

A

高中物理试题分类集 (2003-2017) 王宗民 整理 版权所有 翻印必究 All rights reserved



11 A

12

$$\frac{P_A}{P_B} = \frac{\frac{V^2}{R_A}}{\frac{V^2}{R_B}} = \frac{R_B}{R_A}$$

$$= \frac{P_B \frac{L_B}{A_B}}{P_A \frac{L_A}{A_A}} = 2 \times \frac{1}{2} = 1$$

$A_A = A_B$

C

13

$$V = IR \quad V = IR$$

$$2 = I(10 + 30) \quad = 0.05 \times 30$$

$$I = 0.05 A \quad = 1.5 V$$

$$V_{CA} = 10V + 1.5V = 11.5V \#$$

C

14

$$R = \frac{\rho L}{A} \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$= \frac{\rho L}{nA} \quad \frac{1}{R_T} = \frac{n}{R}$$

$$\frac{V}{R_T} = n \times \frac{nA}{\rho L} \quad R_T = \frac{\rho L}{n^2 A}$$

$$= \frac{1}{n^2} R_0 \#$$

B

15

C

16

$$E = I(R+r) \quad V = IR$$

$$4 = I(2.5 + 1 + 0.5) \quad 1.5 = I \left( \frac{2.5}{100} L \right)$$

$$4 = 4I \quad L = 60 \text{ cm} \#$$

$$I = 1 A$$

B

17 A

18

$$I = nAve$$

$$\frac{V}{R} = nAve$$

$$\frac{VA}{\rho L} = nAve$$

$$v = \frac{V}{ne\rho L}$$

C

19

$$E = I(R+r)$$

$$= V + Ir$$

$$= 12 + (4 \times 0.4)$$

$$= 13.6 V \#$$

D

20

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \quad E = I(R+r)$$

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{12} \quad 12 = I(4+2)$$

$$R = 4 \Omega \quad I = 2 A$$

21

$$V = IR$$

$$12 = 2(2) = I \times 6$$

$$I = 1.33 A$$

C

22

并联 串联

$$E = I(R+r) \quad E = I(R+r)$$

$$1.5 = I(10 + \frac{r}{10}) \quad 1.5 \times 10 = I(10 + 10r)$$

$$I = \frac{15}{100+r} \quad I = \frac{15}{10+10r} \#$$

①带进②

$$\frac{15}{100+r} = \frac{15}{10+10r}$$

$$100+r = 10+10r$$

$$r = 10 \Omega \#$$

C



No. ....

较好的输出。但时间久了,  $r$  变大 ( $3\Omega$  或更大  $I_r$  即变大, 而  $V_R I$  变小, 小到没有可观的输出, 这时干电池就要作废了。不能一直使用至  $V_R$  变为零, 因为  $r$  越来越大, 干电池的大部分输出功率都被内电阻消耗了。

②③  $E = I(R+r)$

$V = IR$

$\frac{1}{R} = \frac{1}{10} + \frac{1}{10}$

$E = I(R+r)$

$24 = I(3+R'+1)$

$6 = I(\frac{30}{100}R')$

$R = 5\Omega$

$12 = I(5+0)$

$24 = \frac{20}{R'}(4+R')$

$I = \frac{20}{R'}$

$I = 2.4 A$

$24 = \frac{80}{R'} + 20$

$R' = 20\Omega$

B

②(a)(i)  $P_T = P_0(1+\alpha\Delta T)$

$= 100 \times 10^{-8} [1 + 0.0004 \times (800 - 273)]$

$= 1.21 \times 10^{-6} \Omega m$

②④  $E_1 - E_2 + I_3 r_2 + I_3 R_3 - I_1 R_1 - I_1 r_1 = 0$

$E_1 - E_2 = I_1 r_1 + I_1 R_1 - I_3 r_2 - I_3 R_3$

D

(ii)  $P = \frac{V^2}{R}$

$600 = \frac{220^2}{R}$

$R = 80.67 \Omega$

作答题

① (a) 新的干电池的内阻很小 (约  $0.1\Omega$ ), 根据公式  $E = IR + Ir \Rightarrow EI = IV_R + I^2 r$  其电功率  $V_R I$  相对来说就较大也即它有

(iii)  $R = \rho \frac{l}{A}$

$80.67 = 1.21 \times 10^{-6} \frac{l}{A}$

$\frac{l}{A} = 6.67 \times 10^7 m^{-1}$

(b)(i)  $E = I(R+r)$

$12 = I(5.5+0.5)$

$I = 2 A$

$R = \rho \frac{l}{A}$

$= P_0(1+\alpha\Delta T) \frac{l}{A}$

$= 100 \times 10^{-8} (1 + 0.0004 \times 30) \times 6.67 \times 10^7$

$= 67.47 \Omega$

(ii)  $P = I^2 R$

$= 2^2 \times 5.5$

$= 22 W$

(b)(i)  $P = I^2 R$

$P = VI$

$10^{-8} = I^2(1)$

$8 = V\sqrt{2}$

$I_R = \sqrt{2}$

$V = 4\sqrt{2}$

(c)(i)  $\frac{1}{R} = \frac{1}{10} + \frac{1}{10+10}$

$E = I(R+r)$

$R = 6\frac{2}{3} \Omega$

$12 = I(6\frac{2}{3} + 0)$

$I = 1.8 A$

$V = I_R R$

$I_R = I_R + I_{R'}$


$4\sqrt{2} = I_R \times 40$

$\sqrt{2} = \frac{\sqrt{2}}{10} + I_{R'}$

$I_R = \frac{\sqrt{2}}{10}$

$I_{R'} = \frac{9\sqrt{2}}{10}$

(ii)

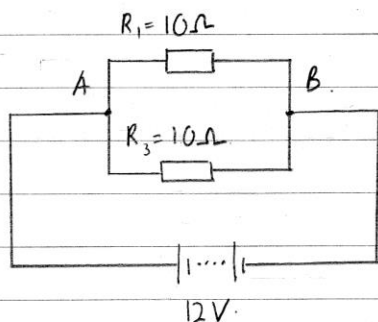

$V = V_R + I_{R'} R'$

$P = V_R I_{R'}$

$4\sqrt{2} = V_R + \frac{9\sqrt{2}}{10} \times 2.5$

$= 2.47 \times \frac{9\sqrt{2}}{10}$

$V_R = 2.47$

$= 3.15 W$

$P = VI \quad P = I^2 R \quad P = \frac{V^2}{R}$

$$(ii) P_{xt} = I_{xt}^2 R_{xt} \quad P = EI$$

$$3.15 = \left(\frac{9\sqrt{2}}{10}\right)^2 R_{xt} \quad 10 = E\sqrt{2}$$

$$R_{xt} = 1.94 \Omega \quad E = 5\sqrt{2}$$

$$E = I(R+r)$$

$$5\sqrt{2} = \frac{9\sqrt{2}}{10}(1.94 + R' + 1)$$

$$R' = 2.62 \Omega \#$$

③ (i) 看回 Graph paper.

$$(ii) I = 1.42; V = 2.88; P = 4.09W$$

$$I = 1.25; V = 3.61; P = 4.51W$$

$$I = 1.13; V = 4.14; P = 4.68W$$

$$I = 1.05; V = 4.52; P = 4.75W \text{ Max.}$$

$$I = 0.97; V = 4.82; P = 4.68W$$

$$I = 0.86; V = 5.31; P = 4.57W$$

$$I = 0.79; V = 5.64; P = 4.46W$$

$$\therefore P_{max} = 4.75W; R = 4\Omega$$

$$(iii) \frac{1}{R} = \frac{1}{4} + \frac{1}{30} \quad V = IR$$

$$R = 3\frac{9}{17} \quad 4.52 = 1.05(3\frac{9}{17} + R_A)$$

$$R_A = 0.78 \Omega \#$$

④ (a)(i)  $E = I(R+r)$


$$12 = I(20+1)$$

$$I = 0.571 A \#$$

(ii)  $E = I(k+r)$

$$12+12 = I(20+2+2)$$

$$I = 1 A \#$$

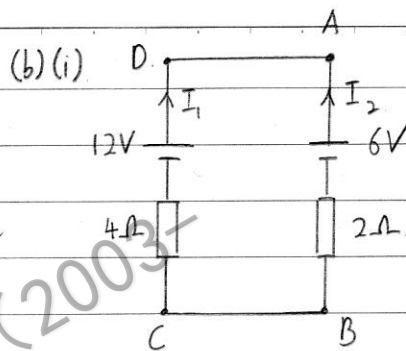


$$V = IR$$

$$12 - 6 = I(4+2)$$

$$I = 1 A \#$$
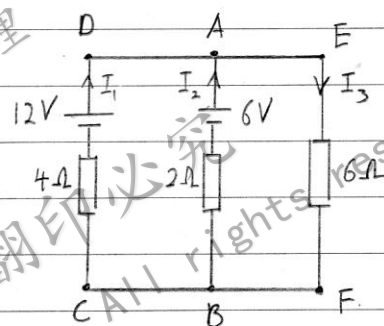
$$\therefore I_1 = 1A; I_2 = -1A; I_3 = 0A$$



节点 A:  $I_1 + I_2 = I_3$

回路 AEFBA:  $6 - 6I_3 + 2I_2 = 0$

$$6 - 6(I_1 + I_2) - 2I_2 = 0$$

$$6 - 6I_1 - 8I_2 = 0 \quad (1)$$

回路 DABCD:  $12 - 6 + 2I_2 - 4I_1 = 0$

$$6 + 2I_2 - 4I_1 = 0$$

$$2I_2 = 4I_1 - 6$$

$$I_2 = 2I_1 - 3 \quad (2)$$

② 带入①

$$6 - 6I_1 - 8(2I_1 - 3) = 0$$

$$6 - 6I_1 - 16I_1 + 24 = 0$$

$$22I_1 = 30$$

$$I_1 = \frac{30}{22} A / 1.4 A \#$$

$$I_2 = 2I_1 - 3$$

$$= 2\left(\frac{30}{22}\right) - 3$$

$$= -\frac{3}{11} A / -0.27 A \#$$

$$I_3 = I_1 + I_2$$


$$= \frac{30}{22} - \frac{3}{11}$$

$$= \frac{12}{11} A / 1.09 A \#$$

⑤ (a)  $V = IR$   
 $8.4 = 5R$   
 $R = 1.68 \Omega$  #

(b)  $R = \frac{\rho L}{A}$   
 $1.68 = \frac{\rho \times 1 \times 100}{\pi (0.01 \div 1000)^2}$   
 $\rho = 5.28 \times 10^{-8} \Omega \cdot m$  #

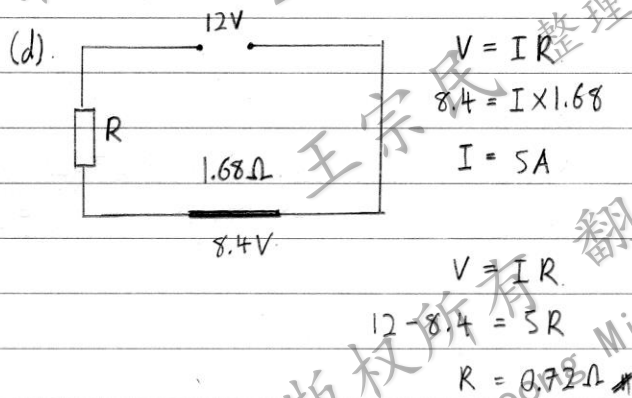(c)  $W = I^2 R t$   
 $= 5^2 \times 1.68 \times 60$   
 $= 2520 J$  #




⑥ (a)  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$   
 $\frac{1}{R} = \frac{1}{12} + \frac{1}{6}$   
 $R = 4 \Omega$   
 $R_T = 10 + 6 + 4 = 20 \Omega$  #

$V = IR$   
 $30 = I(20)$   
 $I = 1.5 A$  #


(b)  $V = IR$   
 $= 1.5 \times 6$   
 $= 9 V$  #  
 $V_{zr} = V_z - V_y$   
 $9 = V_z - 0$   
 $V_z = 9 V$  #

$\therefore$  电容器 C 两极板间的电势差 = 9V #

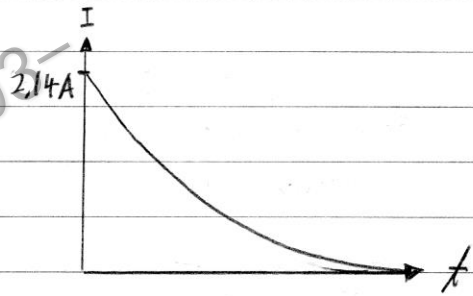
(c)  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$   
 $\frac{1}{R} = \frac{1}{12} + \frac{1}{6}$   
 $R = 4 \Omega$   
 $V = I_{max} R_T$   
 $30 = I_{max} (4 + 10)$   
 $I_{max} = 2.14 A$  #



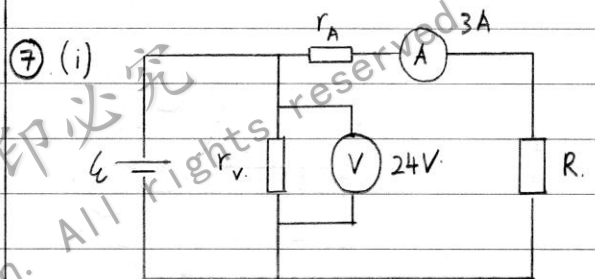(d)  $E = \frac{1}{2} C V^2$   
 $= \frac{1}{2} \times 10 \times 10^{-6} \times 9^2$   
 $= 4.05 \times 10^{-4} J$  #



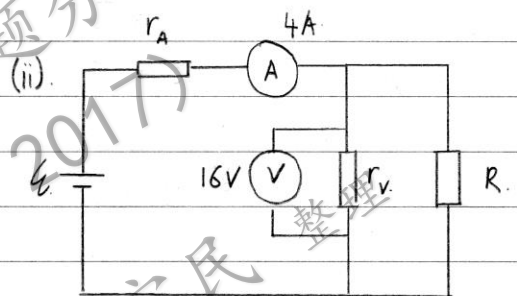$E = I(R + r)$   
 $E = 3(R + r_A)$   
 $24 = 3(R + r_A)$   
 $8 = R + r_A$  ① #



$V = IR$   
 $24 - 16 = 4r_A$   
 $r_A = 2 \Omega$  ②  
 $\frac{1}{R_T} = \frac{1}{r_V} + \frac{1}{R}$   
 $\frac{1}{R_T} = \frac{R r_V}{R + r_V}$   
 $R_T = \frac{R r_V}{R + r_V}$

② 带 ①  
 $8 = R + 2$

$$V = IR$$

$$16 = 4 \left( \frac{Rr_v}{R+r_v} \right)$$

$$16 = 4 \left( \frac{6r_v}{6+r_v} \right)$$

$$4(6+r_v) = 6r_v$$

$$24 + 4r_v = 6r_v$$

$$r_v = 12 \Omega \#$$

$$V = 6 - 20I_1$$

$$= 6 - 20 \times 0.5$$

$$= -4V$$


∴ 伏特表的读数为 4V。

$$(iii) \quad W = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \times 120 \times 10^{-6} \times 4^2$$

$$= 9.6 \times 10^{-4} J \#$$

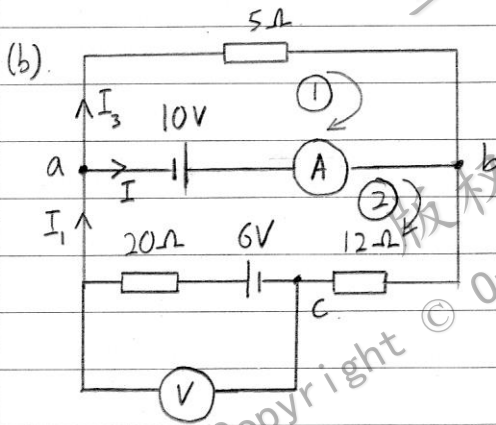3) (a) 基尔霍夫定则包含节点电流定则及回路电压定则。在任一节点上的电流代数和为零，称为节点电流定则。在任一绕行方向上，整个回路的电势的总和为零，称为回路电压定则。



$$(i) \text{ 节点 } a: I_1 = I + I_3$$

$$I = I_1 - I_3$$

$$\text{回路 } \textcircled{1}: -5I_3 - 10 = 0$$

$$I_3 = -2A \# \#$$

(负数代表与图显示的方向相反)

$$\text{回路 } \textcircled{2}: 10 - 12I_1 + 6 - 20I_1 = 0$$

$$-32I_1 = -16$$

$$I_1 = 0.5A \#$$

$$(ii) \quad I = I_1 - I_3$$

$$= 0.5 - (-2)$$

$$= 2.5A$$

∴ 安培表的读数为 2.5A。

$$\textcircled{9} (i) \quad \frac{1}{R'} = \frac{1}{10} + \frac{1}{5+10} \quad R_T = 6\Omega + 5\Omega$$

$$R' = 6\Omega$$

$$= 11\Omega \#$$

$$E = I(R+r)$$

$$I_1 R_1 = I_2 (R_2 + R_3)$$

$$12 = I(11+1)$$

$$10I_1 = I_2(10+5)$$

$$I = 1A$$

$$10(1 - I_2) = 15I_2$$


$$I_2 = 0.4A \#$$

$$V_2 = I_2 R_2$$

$$= 0.4 \times 10$$

$$= 4V \#$$

(ii)

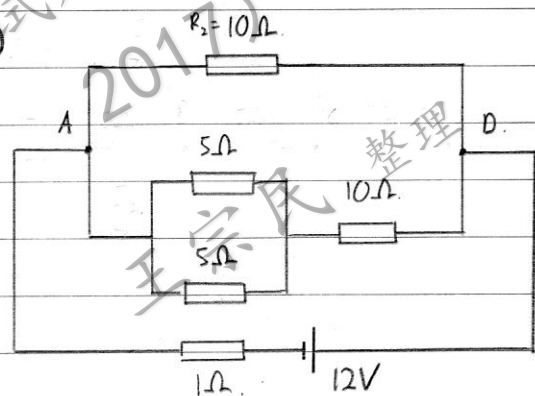

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{2.5+10}$$

$$R_T = 5 \frac{5}{9} \Omega \# / 5.56 \Omega \#$$

$$E = I(R+r) \quad E = I_r + V_2$$


$$12 = I(5\frac{5}{9} + 1) \quad 12 = 1.83 \times 1 + V_2$$

$$I = 1.83 \text{ A} \quad V_2 = 10.17 \text{ V}$$

$$\frac{1}{R_T} = \frac{1}{3} + \frac{1}{5+12} \quad E = I(R+r)$$

$$R_T = 2.55 \Omega \quad 6.3 = I(2.55 + 0.5)$$

$$I = 2.07 \text{ A}$$

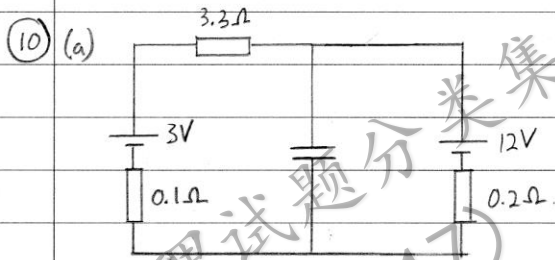

(i)  $E = I(R+r)$

$$12 - 3 = I(3.3 + 0.1 + 0.2)$$


$$I = 2.5 \text{ A}$$

(ii)  $V = IR$        $W = \frac{1}{2} CV^2$

$$= 2.5 \times 0.2 \quad = \frac{1}{2} \times 8 \times 10^{-6} \times (12 - 0.5)^2$$

$$= 0.5 \text{ V} \quad = 5.29 \times 10^{-4} \text{ J}$$

(b) 滑动变阻器的触头在 a 端 1cm 处, 电阻最大,


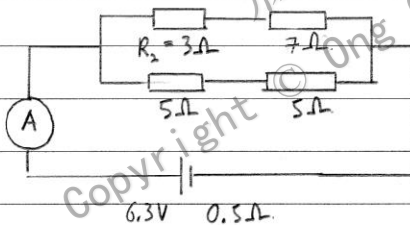


$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{10} \quad E = I(R+r)$$

$$R_T = 5 \Omega \quad 6.3 = I(8 + 0.5)$$

$$I = 1.15 \text{ A}$$

滑动变阻器的触头在 b 端时, 电阻最小。

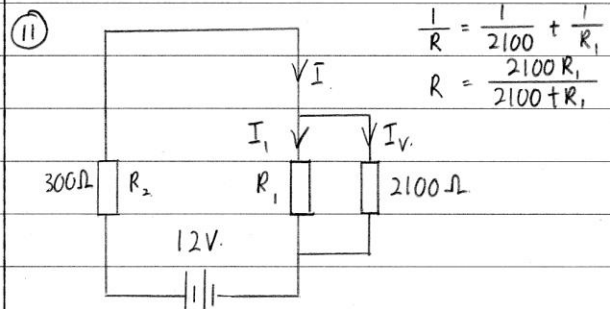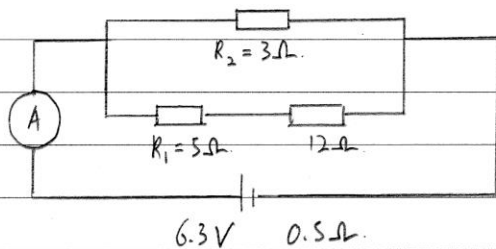

(i)  $V = IR$        $V = I_V R$

$$12 - 8.4 = I \times 300 \quad 8.4 = I_V \times 2100$$

$$I = 0.012 \text{ A} \quad I_V = 0.004 \text{ A}$$

$$I = I_1 + I_V \quad V = I_1 R_1$$

$$0.012 = I_1 - 0.004 \quad 8.4 = 8 \times 10^{-4} R_1$$

$$I_1 = 8 \times 10^{-4} \quad R_1 = 1050 \Omega$$

(ii) 随着量程扩大, 伏特表的内阻也增大, 因而分流变小, 测量到的值变大, 更接近 PQ 间的实际端电压。

⑫ (a) ① 将可变电阻的触头 C 调至接近 Q 处, 接通开关 S, 记下安培表及伏特表的读数。


② 将触头 C 逐步滑向 P, 使电阻变小, 读取 5 组相应的安培表及伏特表读数。

③ 用所得到的数据, 绘出 V-I 坐标图像, 从所绘出的直线图像中, 读取数据, 求出 r。

$$(b)(i) \quad E = I(R+r)$$

$$12 = I(5+1)$$

$$I = 2 \text{ A} \#$$

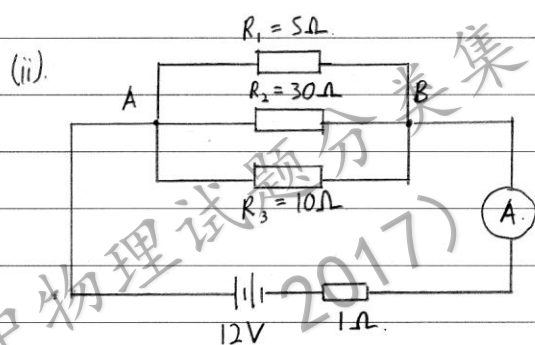

$$\frac{1}{R'} = \frac{1}{5} + \frac{1}{30} + \frac{1}{10}$$


$$R' = 3 \Omega$$

$$E = I(R+r)$$

$$12 = I(3+1)$$

$$I = 3 \text{ A} \#$$

(iii)

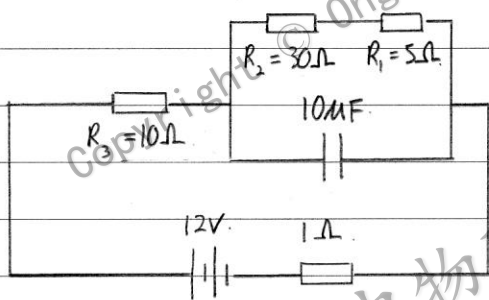

$$E = I(R+r)$$

$$12 = I(10+30+5+1)$$

$$I = 0.261 \text{ A}$$

$$V_c = IR$$

$$= 0.261 \times 35$$

$$= 9.13 \text{ V}$$

$$E = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \times 10 \times 10^{-6} \times 9.13^2$$

$$= 4.17 \times 10^{-4} \text{ J} \#$$

$$(13) \quad \frac{1}{C_T} = \frac{1}{1.5\mu + 4.5\mu} + \frac{1}{3\mu}$$

$$C = 2 \mu\text{F}$$

$$C = \frac{Q}{V}$$

$$2 \times 10^{-6} = \frac{Q}{10}$$

$$Q = 2 \times 10^{-5} \text{ C}$$

$$E = \frac{1}{2} \frac{Q^2}{C}$$

$$= \frac{1}{2} \times \frac{(2 \times 10^{-5})^2}{3 \times 10^{-6}}$$

$$= 6.67 \times 10^{-5} \text{ J} \#$$



